

- \* Oscillators may be broadly divided into two categories: Harmonic oscillators and Relaxation oscillators.
- \* Both types can include Active devices such as BJTs, FETs, and op-amps, and passive components such as resistors, inductors and capacitors.
- \* In Harmonic oscillators, the energy always flows in one direction - from the active to passive components.
- \* In Relaxation oscillators, the energy is exchanged between the active and passive components.
- \* In harmonic oscillators, the frequency of oscillations is determined by the feedback path.
- \* In relaxation oscillators, the frequency is determined by time constants - specifically, the charge and discharge time constants during the exchange of energy.
- \* Harmonic oscillators can develop low-distortion sinusoidal output waveforms, but relaxation oscillators can only generate non-sinusoidal wave-forms such as ~~saw~~ sawtooth, square or triangular.

Operation of oscillator:

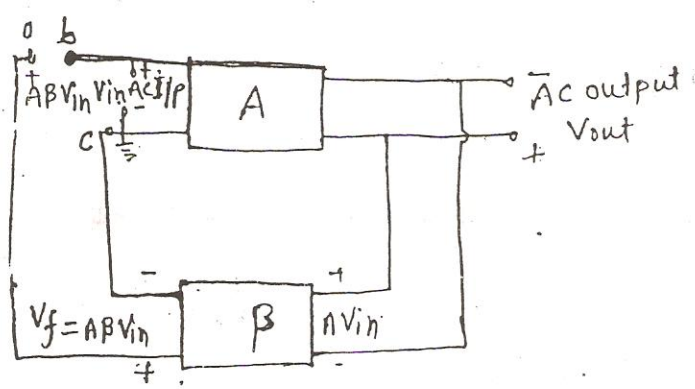


Fig 1

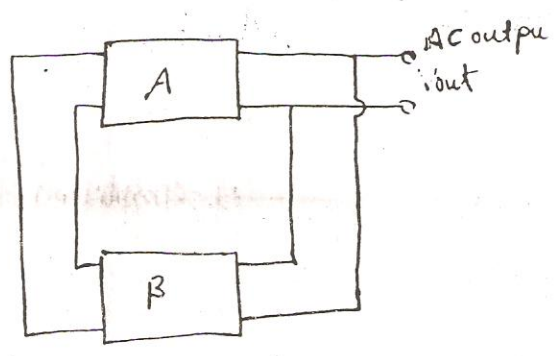


Fig 2

signal will build up, shown in fig. (d)  
\* if  $A\beta$  is equal to unity,  $A\beta V_{in}$  equals  $V_{in}$  and the output signal is a steady sine wave, shown in fig (e)

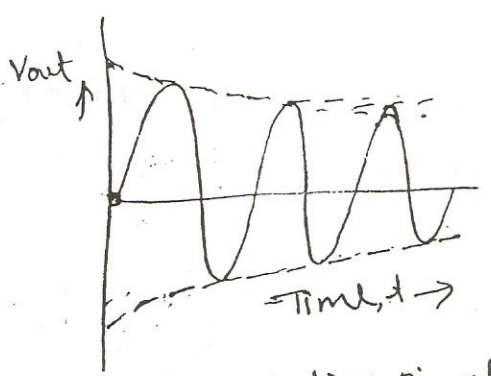


fig (c) oscillations Die out


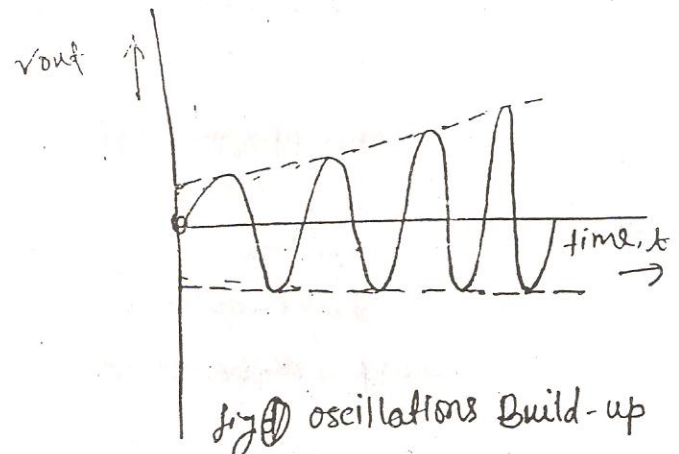


fig (d) oscillations Build-up

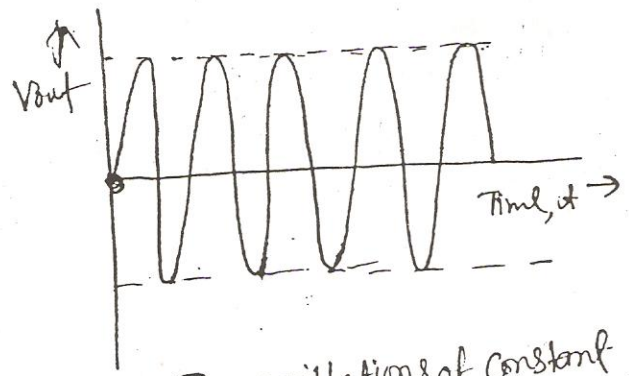

(e) Oscillations of constant Amplitude. (Sine wave)

L-C oscillators:- which use inductance-capacitance (L-C) circuits as their tank or oscillatory circuits are called L-C os. The L-C oscillators are very popular for generating high-freq outputs. (e.g. 10kHz to 100MHz). There is a large variety of L-C oscillators such as tuned-collector oscillators, tuned-base oscillators, colpitts oscillators, Hartly oscillators, clapp oscillators, crystal oscillators etc.