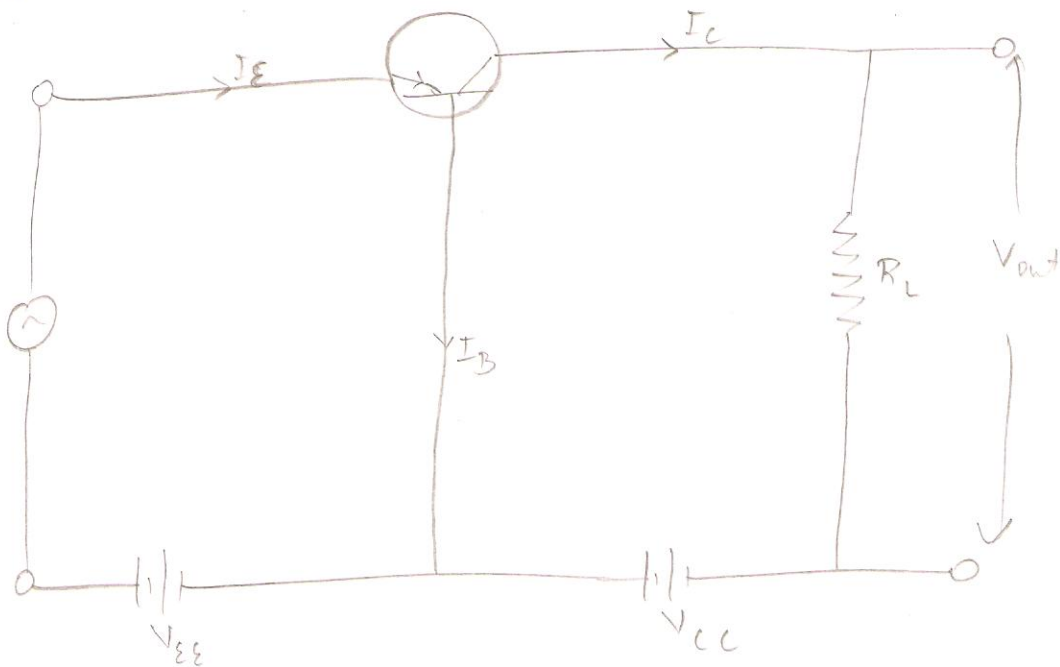


Que-7 (i) Transistor as an amplifier.

(ii) Transistor as an oscillator.

Ans (i) Transistor as an amplifier →



$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$\Delta I_C = \alpha \Delta I_E$$

$$\Delta V_o = R_L \Delta I_C$$

$$= R_L \alpha \Delta I_E$$

$$A = \frac{\Delta V_o}{\Delta V_i}$$


$$\Delta V_i = \delta_e \Delta I_E$$

$$A = \frac{R_L \alpha \Delta I_E}{\delta_e \Delta I_E} = \frac{\alpha R_L}{\delta_e}$$

Emitter as i/p terminal & collector as o/p terminal transistor is biased to operate in active region weak signal is applied b/w emitter base current & o/p is taken across R_L in collector base circuit for faithful ampli. V_{EE} is connected to i/p. Small change in i/p produces appreciable change in emitter I. As i/p circuit has no resistance. Change in I_E changes I_{CE} when

I_e flows through R_L a large voltage is developed.

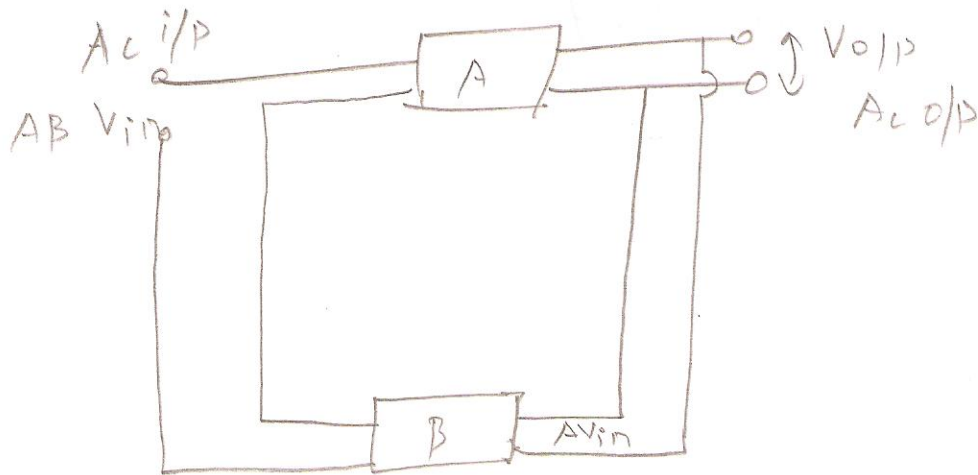(ii) Operation of Oscillator: \rightarrow





$$V_f = ABV_{in}$$



$$A = \frac{V_{out}}{V_{in}}$$

(a)
$$\beta = \frac{V_f}{AV_{in}}$$

$$V_f = \beta AV_{in}$$

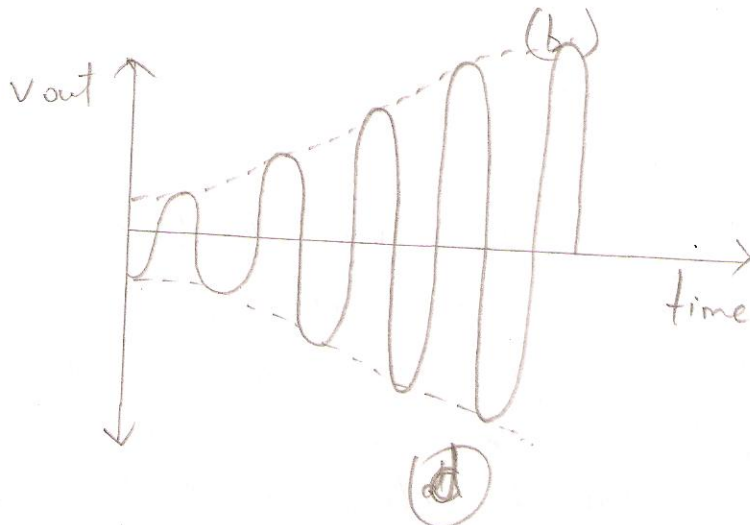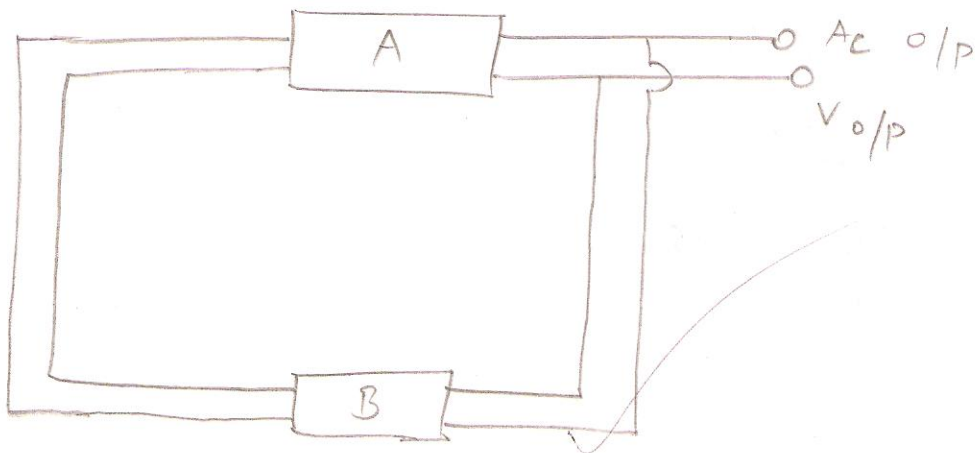

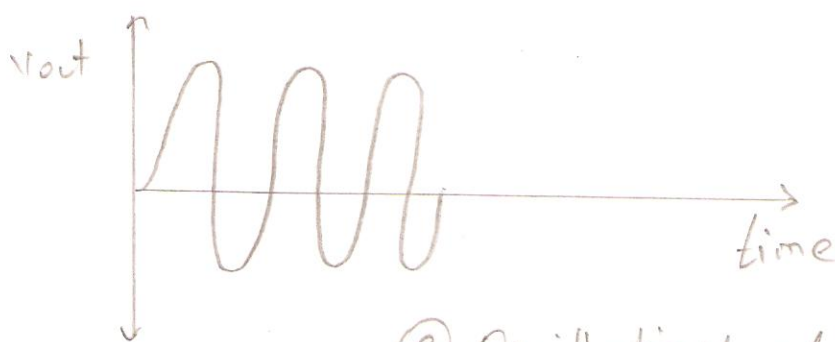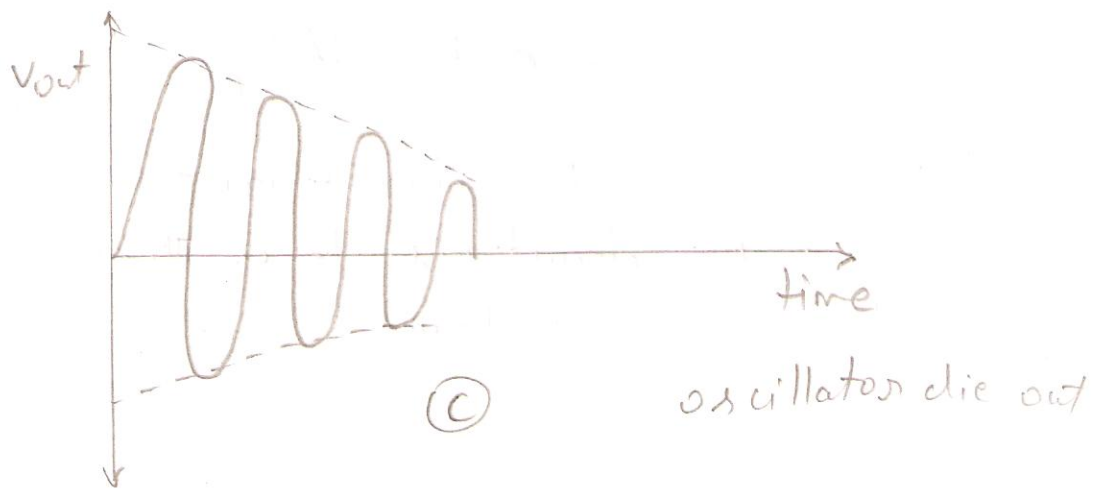oscillator ~~built up~~ ~~built up~~ die out



(e) Oscillations of Constant amplitude.

Use of the feedback is required in a oscillator that result in a feedback amplifier having close loop gain > 1 in fig (a). A feedback circuit having V_{in} as the voltage of $A_{i/p}$ driving i/p terminals V_c of an amplifier having volt. gain 'A'. $A_{out} = AV_{in}$. The voltage drives a feedback circuit that is a resonance circuit max. Feedback is at one freq. feedback voltage returning to point 'A' is given by eqⁿ $V_f = ABV_{in}$ where β is the gain of feedback network. If the phase shift through amp^r & feedback circuit is zero then ABV_{in} is in phase with the i/p signal V_{in} that drives the i/p terminals connecting a to b & simultaneously removing source voltage V_{in} than feedback voltage ABV_{in} drives of an amp^r as in fig (B) If AB is less than unity ABV_{in} is less than V_{in} .

Then o/p signal will die out as in fig (c) As AB is greater than unity o/p will built up as

in fig (d). As $AB=1$ then $ABV_{in} = V_{in}$ & o/p is the steady
sine wave as in figure (e) to fulfill.

For sustained oscillation
are 0 loop gain of the circuit must be equal to '1'.

Phase shift around the circuit must be 0. These two conditions
are called back person criteria.

